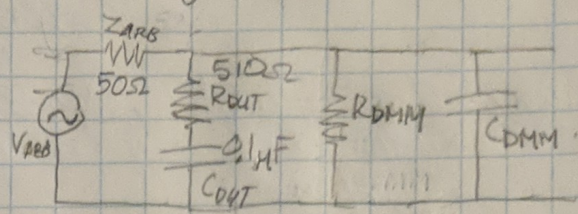


Lab VIEW ATE Homework

a) Input frequency DUT Input Voltage (RMS)

50 Hz	1.01351 V
500 Hz	1.01215 V
5000 Hz	1.01174 V
50000 Hz	1.01071 V

b) Diagram



c)

$$V_{out}(j\omega) = V_{ABB} \frac{(R_{OUT} + \frac{1}{sC_{OUT}}) \parallel R_{DMM} \parallel \frac{1}{sC_{DMM}}}{Z_{ABB} + (R_{OUT} + \frac{1}{sC_{OUT}}) \parallel R_{DMM} \parallel \frac{1}{sC_{DMM}}}$$

$$= V_{ABB} \frac{\frac{A}{B}}{\frac{A}{B} + Z_{ABB}} = V_{ABB} \frac{\frac{A}{B}}{\frac{A + Z_{ABB}B}{B}} = V_{ABB} \frac{A}{A + Z_{ABB}B}$$

$s = j\omega$ at Steady State

$$= \frac{1}{\frac{1}{R_{OUT} + \frac{1}{sC_{OUT}}} + \frac{1}{R_{DMM}} + sC_{DMM}}$$

$$= \frac{sC_{OUT}}{s(R_{OUT}C_{OUT} + 1) + \frac{R_{DMM}}{R_{OUT}C_{OUT} + 1} + sC_{DMM}}$$


$$= \frac{sR_{DMM}C_{OUT}}{sR_{DMM}C_{OUT} + 1 + sR_{DMM}C_{DMM}}$$

$$= \frac{sR_{DMM}R_{OUT}C_{OUT} + R_{DMM}}{s^2R_{DMM}R_{OUT}C_{DMM}C_{OUT} + s(R_{DMM}C_{DMM} + R_{OUT}C_{OUT}) + R_{DMM}}$$

sub $\Rightarrow \frac{A}{B}$


$$V_{out}(j\omega) = V_{ABB}(j\omega) \frac{j\omega R_{DMM}R_{OUT}C_{OUT} + R_{DMM}}{j\omega Z_{ABB}R_{DMM}C_{DMM}C_{OUT} + j\omega(R_{DMM}R_{OUT}C_{OUT} + Z_{ABB}(R_{DMM}C_{DMM} + R_{OUT}C_{OUT}) + R_{DMM}) + Z_{ABB}}$$

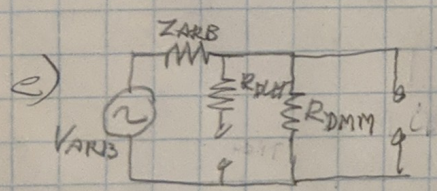d) $\lim_{\omega \rightarrow 0} V_{out}(j\omega) = \frac{V_{ABB}(DC) R_{DMM}}{R_{DMM} + Z_{ABB}}$



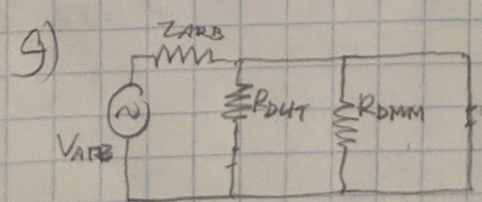f) $\lim_{\omega \rightarrow \infty} V_{out}(j\omega)$ by l'Hopital's $\lim_{\omega \rightarrow \infty} V_{ABB}(j\omega) \frac{R_{DMM}R_{OUT}C_{OUT}}{2j\omega R_{DMM}R_{OUT}C_{DMM}C_{OUT}Z_{ABB} + R_{DMM}R_{OUT}C_{OUT} + Z_{ABB}(R_{DMM}C_{DMM} + R_{OUT}C_{OUT}) + R_{DMM}}$

l'Hopital's again $= \lim_{\omega \rightarrow \infty} V_{ABB}(j\omega) \frac{0}{2R_{DMM}R_{OUT}C_{DMM}C_{OUT}Z_{ABB}} = 0$



h) Since the arbitrary function generator is in hi-Z mode the DC circuit is a simple voltage divider between Z_{ABB} and R_{DMM} . Capacitors act as open circuits at DC. The capacitors decrease in impedance as frequency increases according to the equation $X_C = \frac{1}{j\omega C}$ at steady state. As frequency becomes arbitrarily large the capacitor impedance approaches 0, leaving the Multimeter acting as a short circuit.